



ÇUKUROVA
ÜNİVERSİTESİ

Department
of
Computer Engineering

CEN 263

Digital Design

Autumn 2024

Lecture 2

Announcements


- Website:



Week 2 Outlines

- Combinational logic
- Boolean algebra
- Simplification of Boolean expressions


Where are we now?

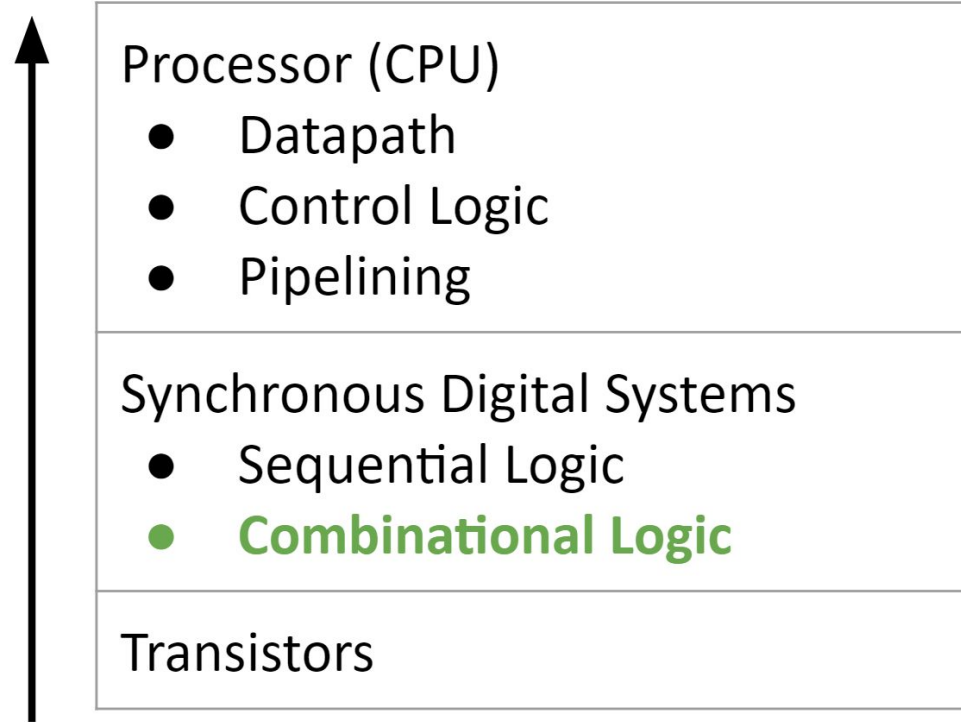

Note: Transistors will not be in scope for exams.

Logic Gates

 - Operators with:
 - One or more 1-bit inputs
 - One 1-bit output
- Can be built out of transistors
- Can be represented as:
 - A block in a circuit diagram
 - A truth table, listing the output for every possible input
 - A Boolean algebra expression
- Used to perform bitwise operations
 - Recall: We saw bitwise operations (NOT, OR, AND, XOR)



NOT

- One 1-bit inputs, labeled A
- One 1-bit output, labeled Out
- Can be represented as:



A diagram

$$\text{Out} = \bar{A}$$


An algebraic expression

A	Out
0	1
1	0

A truth table

OR

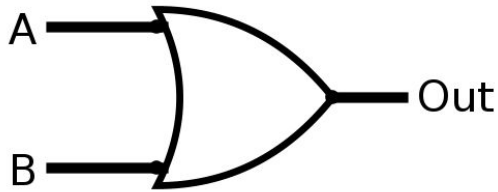
- Two 1-bit inputs, labeled A and B
- One 1-bit output, labeled Out
- Can be represented as:



A diagram

$$\text{Out} = A + B$$

An algebraic expression

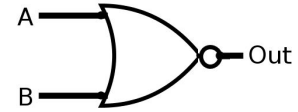


NOR gate looks like this.

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

A truth table

AND

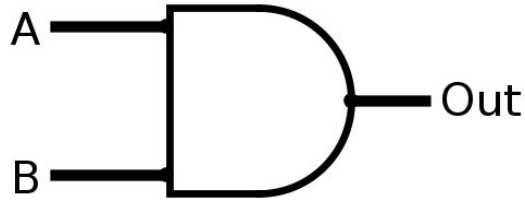- Two 1-bit inputs, labeled A and B
- One 1-bit output, labeled Out
- Can be represented as:



A diagram

$$\text{Out} = AB$$


An algebraic expression

A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

A truth table

XOR

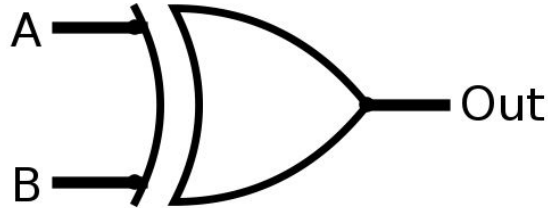- Two 1-bit inputs, labeled A and B
- One 1-bit output, labeled Out
- Can be represented as:



A diagram

$$\text{Out} = \bar{A}B + \bar{B}A$$

An algebraic expression

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0


A truth table

Combinational Logic

- We can combine logic gates to make larger circuits
 - One or more inputs
 - One or more outputs
 - Perform more complicated logic operations
- These circuits can also be represented as
 - A block in a circuit diagram
 - A truth table, listing the output for every possible input
 - A Boolean algebra expression

Mystery Circuit #1

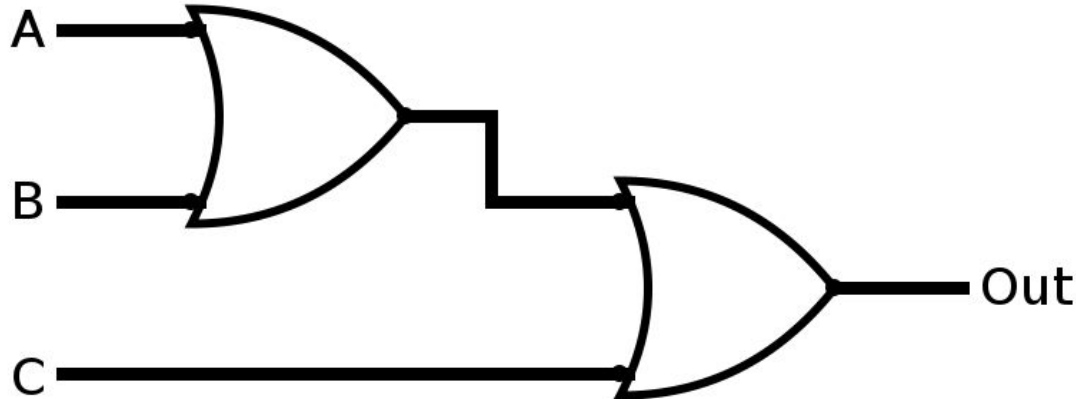- Three 1-bit inputs, labeled A, B, C
- One 1-bit output, labeled Out




Let's try to write the truth table from the circuit diagram.

How many rows are in the truth table?
(Hint: How many unique inputs are there?)

Mystery Circuit #1

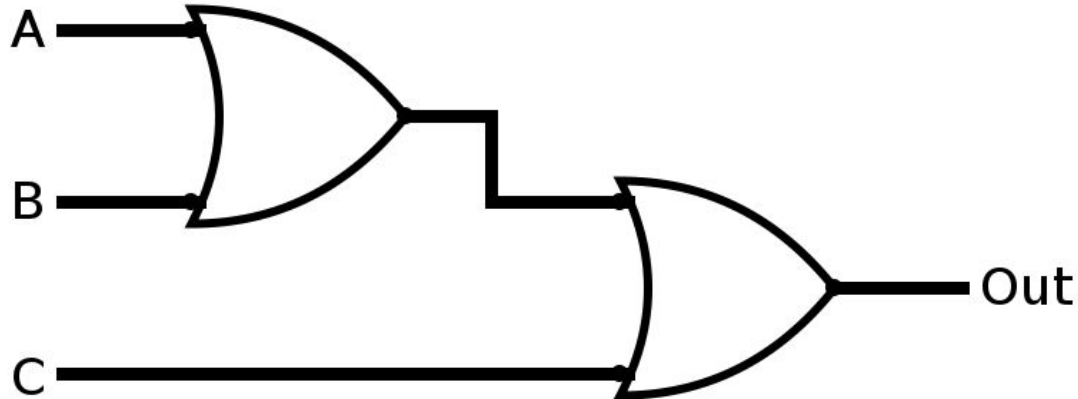- Three 1-bit inputs, labeled A, B, C
- One 1-bit output, labeled Out




A	B	C	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Try inputs on the circuit
to fill out the truth table!

Mystery Circuit #1

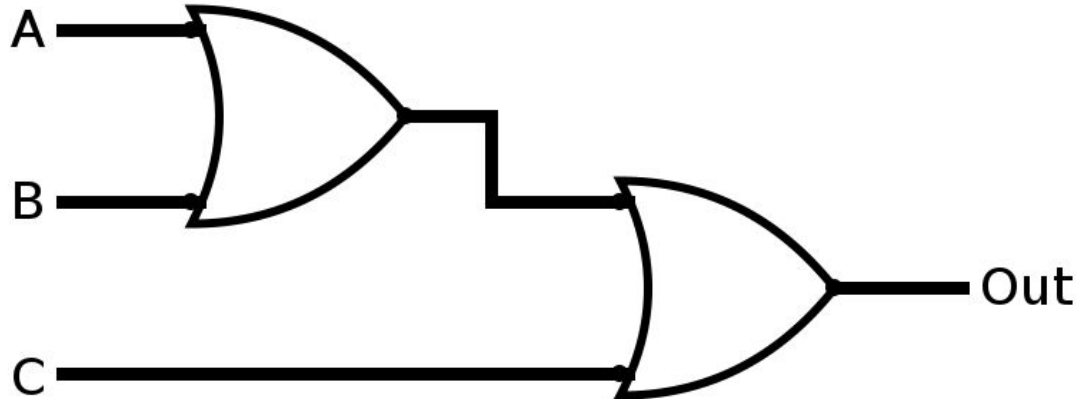- Three 1-bit inputs, labeled A, B, C
- One 1-bit output, labeled Out




A	B	C	Out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Let's write the algebraic expression from the circuit.

Mystery Circuit #1

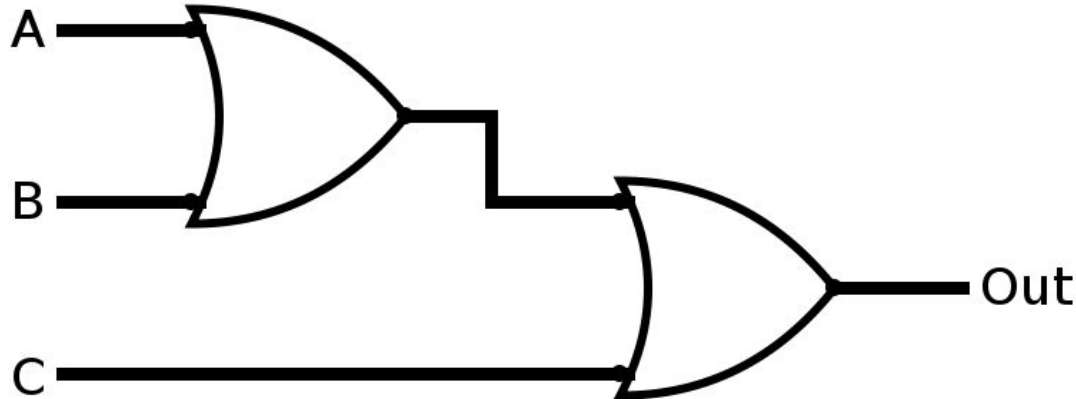- Three 1-bit inputs, labeled A, B, C
- One 1-bit output, labeled Out





A	B	C	Out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{Out} = (A + B) + C$$

Mystery Circuit #1: 3-way OR

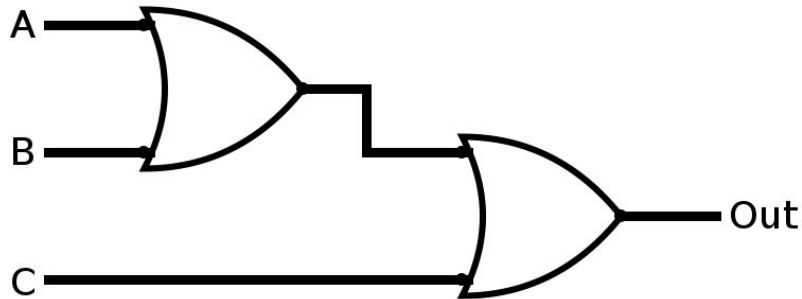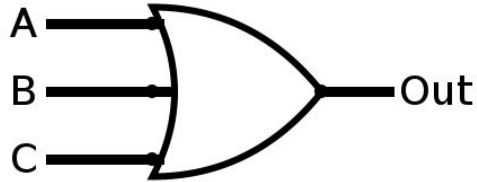
- Intuitively: Outputs 1 when at least one of the inputs is 1
- Sometimes drawn like this:



A	B	C	Out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{Out} = (A + B) + C$$

Converting Between Representations

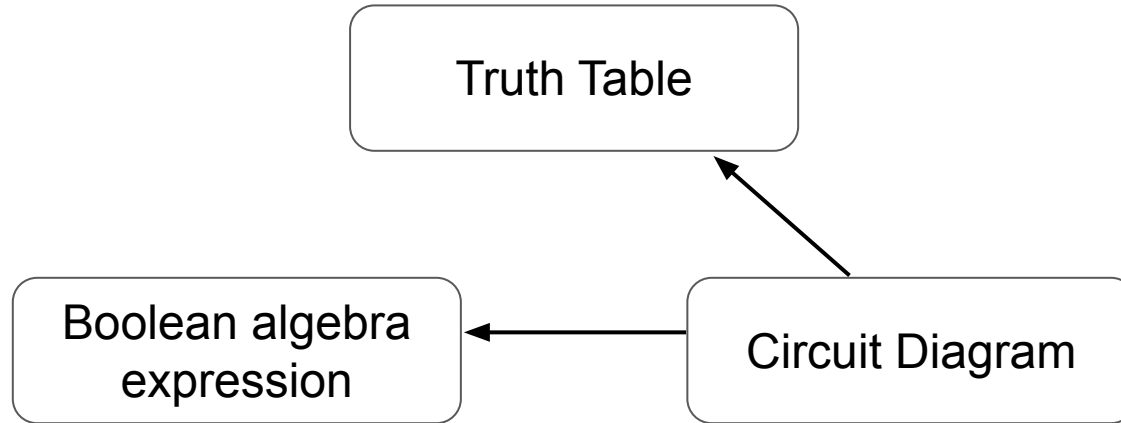

We converted a circuit diagram to a truth tables and algebraic expression.

Can we convert between the other representations too?

Mystery Circuit #2


- Three 1-bit inputs, labeled A, B, C
- One 1-bit output, labeled Out

Given the algebraic expression, let's draw the circuit diagram.

$$\text{Out} = AB + BC + AC$$

Mystery Circuit #2

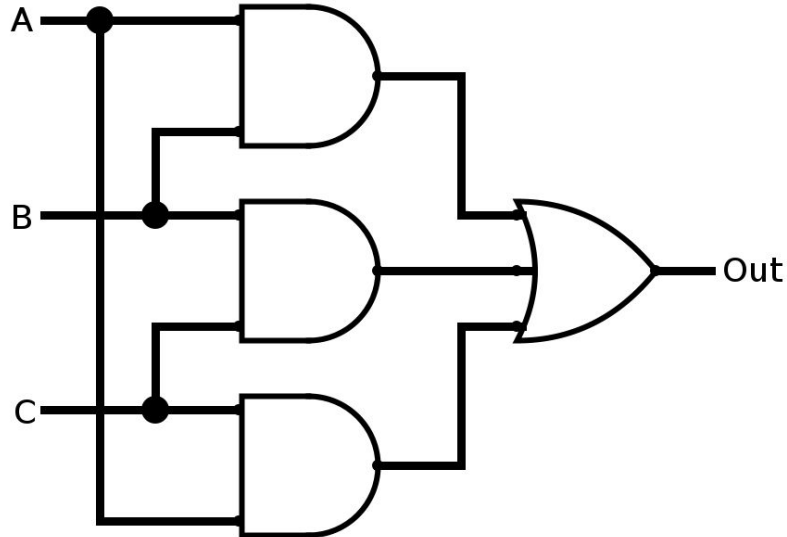- Three 1-bit inputs, labeled A, B, C
- One 1-bit output, labeled Out



$$\text{Out} = AB + BC + AC$$

Mystery Circuit #2

- Three 1-bit inputs, labeled A, B, C
- One 1-bit output, labeled Out


Given the algebraic expression, let's write the truth table.

A	B	C	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$$\text{Out} = AB + BC + AC$$

Mystery Circuit #2

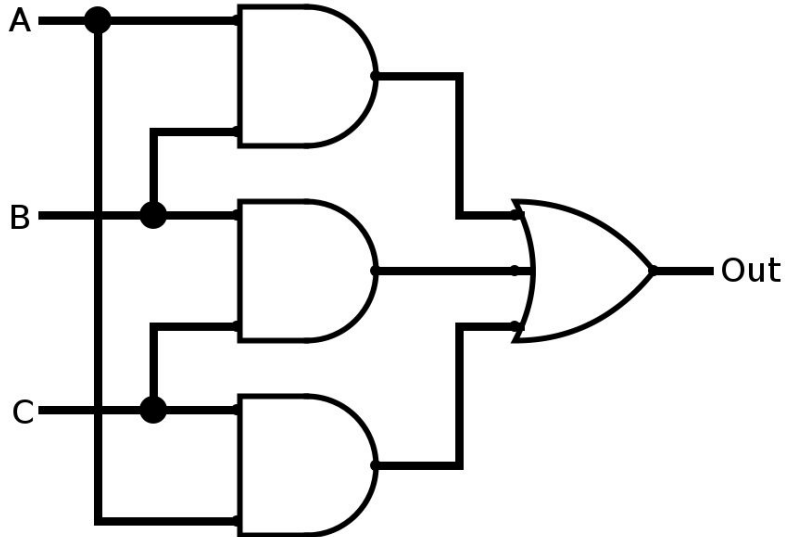- Three 1-bit inputs, labeled A, B, C
- One 1-bit output, labeled Out




A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{Out} = AB + BC + AC$$

Mystery Circuit #2: Majority Circuit

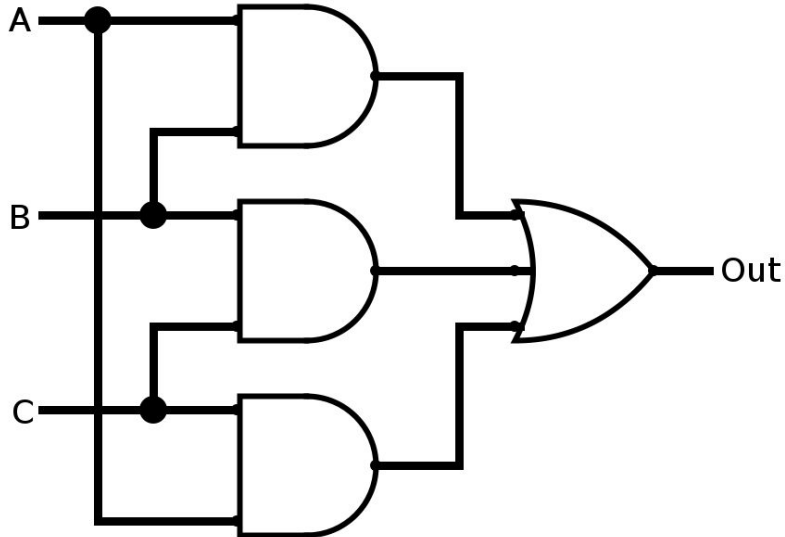
- Intuitively: Outputs the most common value (0 or 1) among the three inputs



A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{Out} = AB + BC + AC$$

Converting Between Representations

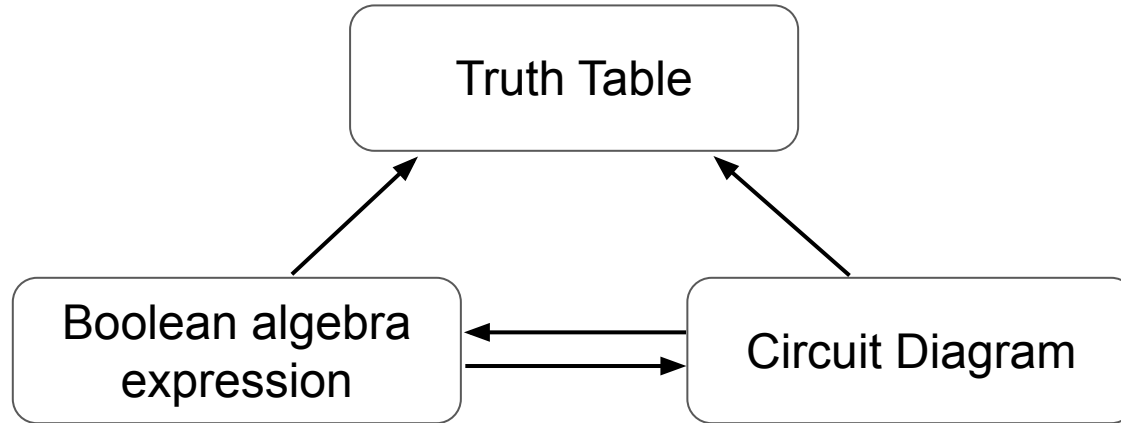


We just converted algebraic expressions to truth tables and circuit diagrams.

Before we see the next conversion, let's talk a bit more about Boolean algebra.

Boolean Algebra

History of Boolean Algebra

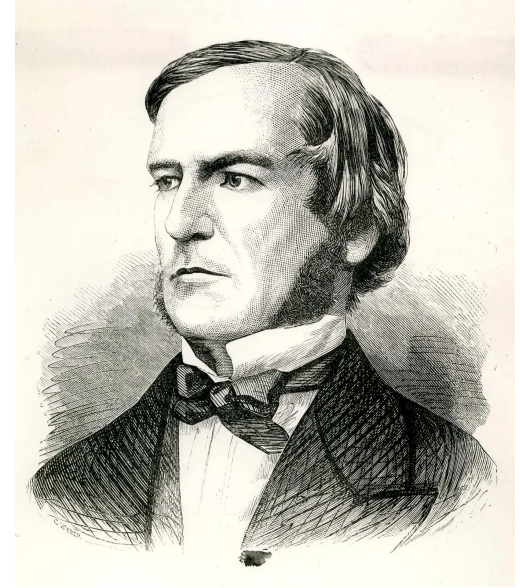- Early computer designers built ad hoc circuits from switches
- Began to notice common patterns in their work: ANDs, ORs, ...
- Master's thesis (by Claude Shannon, 1940) made link between work and 19th century mathematician George Boole
- Called it “Boolean Algebra” in his honor



George Boole

Boolean Algebra Operations

- Recall the Boolean algebra operations from earlier
 - We can compute these operations with logic gates

Operation	Notation
A and B	AB
A or B	$A + B$
not A	\bar{A}

Note: There are a variety of accepted symbols used for these operations.

Simplifying Boolean Algebra

- Given a complicated Boolean algebra expression, we can use some rules to simplify them
 - Useful way to simplify circuits: convert to Boolean algebra, simplify, and convert back
 - Simplifying circuits = less hardware

Laws of Boolean Algebra

Name	AND Form	OR form
Commutative	$AB = BA$	$A + B = B + A$
Associative	$AB(C) = A(BC)$	$A + (B + C) = (A + B) + C$
Identity	$1A = A$	$0 + A = A$
Null	$0A = 0$	$1 + A = 1$
Absorption	$A(A + B) = A$	$A + AB = A$
Distributive	$(A + B)(A + C) = A + BC$	$A(B + C) = AB + AC$
Idempotent	$A(A) = A$	$A + A = A$
Inverse	$A(\bar{A}) = 0$	$A + \bar{A} = 1$
De Morgan's	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}(\bar{B})$

Boolean Algebra Simplification Example

$$\begin{aligned}y &= ab + a + c \\&= ab + a(1) + c && \text{Identity} \\&= a(b+1) + c && \text{Distributive} \\&= a(1) + c && \text{Null} \\&= a + c && \text{Identity}\end{aligned}$$

Sum-of-Products

- Given a truth table, how can we convert it to a Boolean algebra expression?
- Idea: Look for every row where the output is 1
 - For Out=1, we either have:
 - (A=0 and B=0 and C=1), or
 - (A=1 and B=0 and C=1), or
 - (A=1 and B=1 and C=1)
- In Boolean algebra: $(\bar{A})(\bar{B})(C) + (A)(\bar{B})(C) + (A)(B)(C)$
- This is called the sum-of-products form
 - For each row where Out=1, create one product (AND the inputs together)
 - Then take the sum of all the products (OR the products together)

A	B	C	Out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Mystery Circuit #3

- Three 1-bit inputs, labeled A, B, S
- One 1-bit output, labeled Out

Given the truth table, let's write the algebraic expression.

Strategy: Start with sum-of-products form, then simplify with Boolean algebra laws.

A	B	S	Out
0	0	0	0
1	0	0	1
0	0	1	0
1	0	1	0
0	1	0	0
1	1	0	1
0	1	1	1
1	1	1	1

Mystery Circuit #3

- Three 1-bit inputs, labeled A, B, S
- One 1-bit output, labeled Out

$$\begin{aligned}\text{Out} &= (a)(\bar{b})(\bar{s}) + (a)(b)(\bar{s}) + (\bar{a})(b)(s) + abs \\ &= ((a)(\bar{b}) + ab)(\bar{s}) + ((\bar{a})(b) + ab)s \\ &= ((a)(\bar{b} + b))(\bar{s}) + ((\bar{a} + a)(b))s \\ &= (a(1))(\bar{s}) + ((1)b)s \\ &= a(\bar{s}) + bs\end{aligned}$$

A	B	S	Out
0	0	0	0
1	0	0	1
0	0	1	0
1	0	1	0
0	1	0	0
1	1	0	1
0	1	1	1
1	1	1	1

Mystery Circuit #3

- Three 1-bit inputs, labeled A, B, S
- One 1-bit output, labeled Out


Given the simplified algebraic expression, we can draw a circuit diagram with fewer logic gates (compared to drawing a diagram from sum-of-products form).

A	B	S	Out
0	0	0	0
1	0	0	1
0	0	1	0
1	0	1	0
0	1	0	0
1	1	0	1
0	1	1	1
1	1	1	1

$$\text{Out} = (A)(\overline{S}) + (B)(S)$$

Mystery Circuit #3

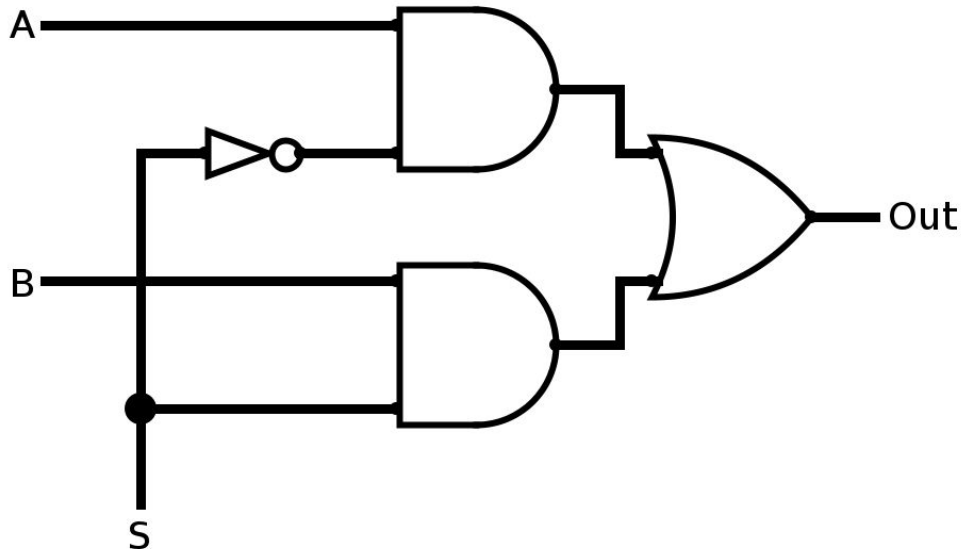- Three 1-bit inputs, labeled A, B, S
- One 1-bit output, labeled Out




A	B	S	Out
0	0	0	0
1	0	0	1
0	0	1	0
1	0	1	0
0	1	0	0
1	1	0	1
0	1	1	1
1	1	1	1

$$\text{Out} = (A)(\bar{S}) + (B)(S)$$

Mystery Circuit #3: Multiplexer (MUX)

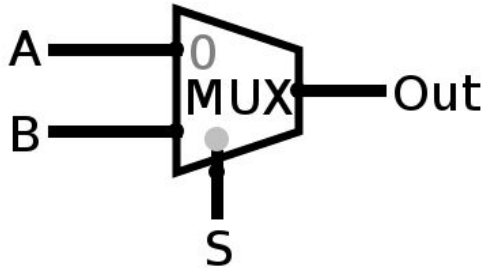
- Intuitively:
 - If S is 0, output the value in A.
 - If S is 1, output the value in B.
 - S is the “select” bit
- Usually drawn like this:



A	B	S	Out
0	0	0	0
1	0	0	1
0	0	1	0
1	0	1	0
0	1	0	0
1	1	0	1
0	1	1	1
1	1	1	1

$$\text{Out} = (A)(\bar{S}) + (B)(S)$$

Converting Between Representations

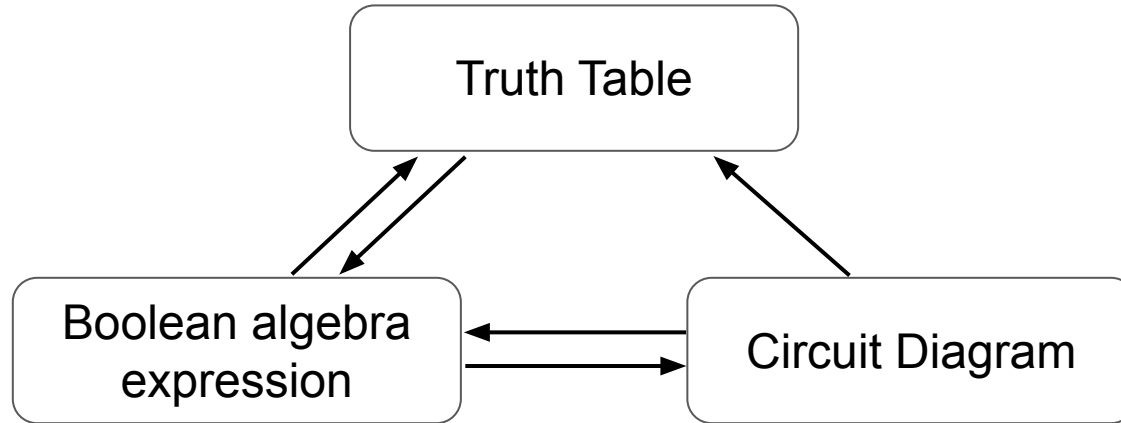

Now, we can convert truth tables to algebraic expressions.

Adders



32-bit Adder

- Inputs:
 - 32-bit input A
 - 32-bit input B
- Outputs:
 - 32-bit output Sum
- How many rows in the truth table?
 - 2^{32} possible inputs for each of A and B
 - 2^{64} possible inputs in total
- Can we build this more efficiently?
 - Yes - connect smaller building blocks together!

1-bit Adder

How do we add binary numbers by hand?

$$\begin{array}{rcccc} & 0 & 0 & 1 & 0 \\ + & 0 & 1 & 1 & 1 \\ \hline \end{array}$$

1-bit Adder

Consider the inputs and outputs in one column:

	(1)	(1)	(0)	
	0	0	1	0
+	0	1	1	1
<hr/>				
	1	0	0	1

Inputs:

- 0, 1: Bits being added
- (1): Carry-in bit

Outputs:

- 0: Sum
- (1): Carry-out bit


1-bit Adder

- Three 1-bit inputs, labeled A, B, C_{in}
- Two 1-bit outputs, labeled Sum and C_{out}

A	B	C_{in}	Sum	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

1-bit Adder

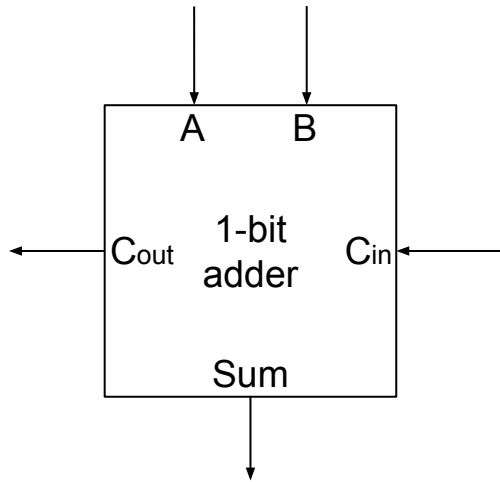- Three 1-bit inputs, labeled A, B, C_{in}
- Two 1-bit outputs, labeled Sum and C_{out}




A	B	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$C_{out} = BC_{in} + AC_{in} + AB$$

$$Sum = A \oplus B \oplus C_{in}$$

n -bit Adder

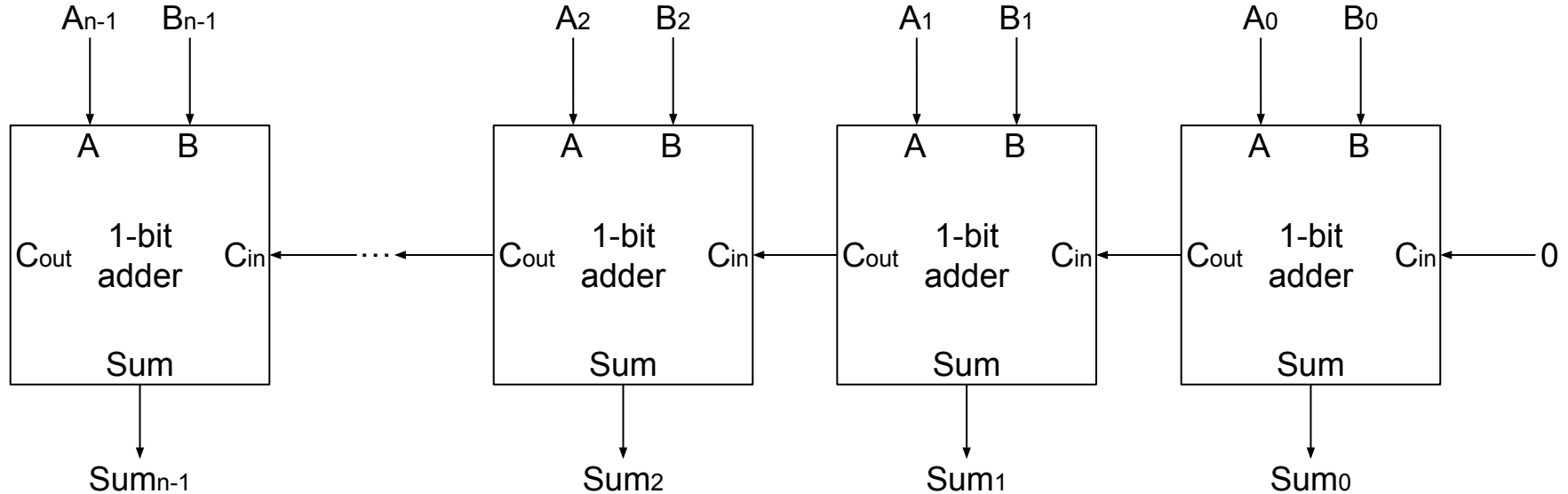- Idea: Chain n 1-bit adders together to add n -bit numbers together



End of Week 2!

Do not go home, we'll have another lecture...